 


# lecture 5


## Sequential circuits I

last week



- signals carried on wires
- gate operations take time (e.g. carries in addition)

this week

 


- Combinational circuits + memory
- Synchronized by a discrete clock C


## Memory (2 kinds)

- write it down
- repeat to yourself (feedback)


## Feedback

 

A	Y
0	0
1	0 or 1
0 → 1	0
1 → 0	0

 

A	Y
0	0 or 1
1	1
0 → 1	1
1 → 0	1

 



A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

A	Y
0	0 ↔ 1 oscillate
1	0

Today


- RS latch
- clocked RS latch
- D latch
- D flip flop, T flip flop
- register

RS latch  
(‘reset’ 0, ‘set’ 1)

  

R	S	Q	Q'
0	0	hold previous values	
0	1	1	0
1	0	0	1
1	1	0	0

“Clock”

 


• doesn't count (just goes ON, OFF, ...)

• electronic implementation not discussed

• typical clock speed today is  
3 GHz ( $10^9$  cycles/sec)

Clocked RS latch

 


C=0

R	S	Q	Q'
0	0	hold	
0	1	1	0
1	0	0	1
1	1	0	0

C=1

R	S	Q	Q'
0	0	hold	
0	1	1	0
1	0	0	1
1	1	0	0

### Example

 


$C=0$

R	S	Q	Q'
0	0	0	1
1	0	0	1
0	1	1	0
1	1	hold	hold

$C=1$

R	S	Q	Q'
0	0	hold	hold
1	0	0	1
0	1	1	0
1	1	0	1

### D latch ("D" for data)


 


What does this circuit do?

when  $C=1$ ,  $D=1 \Rightarrow Q=1$   
 $D=0 \Rightarrow Q=0$

When  $C=0$ , hold values of  $Q, \bar{Q}$

### D latch

  


$C=0 \Rightarrow$  read only


$C=1 \Rightarrow$  read and write

- We can hold values in D latches when  $C=0$ .
- But when  $C=1$ , the circuits are open.
- This becomes a problem when we want feedback in circuits containing D latches

$$x = x + y$$

 

### D flip flop

 



$C=1 \Rightarrow$

- write D into first D latch
- Q holds previous value



$C=0 \Rightarrow$

- stop writing into 1<sup>st</sup> D latch
- copy value from 1<sup>st</sup> to 2<sup>nd</sup> D latch, Q takes (possibly) different value

## D flip flop (falling edge triggered)

  

## D flip flop (rising edge triggered)

  


- Clock cycle is long enough to allow all gates to stabilize.

- Clock synchronizes all flipflops, allowing us to treat time as a sequence of discrete R/W steps (hence "sequential circuit")

- From now on, ignore all variations within a clock cycle (e.g. carries in adder)
 
## Register (set of flip flops that are grouped together)



## Shift register (falling edge)

