

# lecture 4

## Combinational logic

### Last lecture

- truth tables

$$Y = f(A, B, \dots)$$

• sums of products

- logical gates & circuits



## Arithmetic Circuits

$$\begin{array}{r} C_{n-1} \dots C_2 C_1 C_0 \\ A_{n-1} \dots A_2 A_1 A_0 \\ + B_{n-1} \dots B_2 B_1 B_0 \\ \hline S_{n-1} \dots S_2 S_1 S_0 \end{array}$$

Note

•  $C_0 = 0$

•  $A, B$  could be positive or negative

Sum of products?  $\Rightarrow$  fast 😊

$B_{31} A_{31} \dots B_1 A_1 B_0 A_0$	$S_{31} \dots S_2 S_1 S_0$
$2^{32 \cdot 2}$ rows	

$\sim 2^{2 \times 32}$  gates  $\Rightarrow$  big 😞

$$\begin{array}{r} C_{n-1} \dots C_2 C_1 \\ A_{n-1} \dots A_2 A_1 A_0 \\ B_{n-1} \dots B_2 B_1 B_0 \\ \hline S_{n-1} \dots S_2 S_1 S_0 \end{array}$$

$A_0 B_0$	$S_0 C_1$
0 0	0 0
0 1	1 0
1 0	1 0
1 1	0 1


$$S_0 = A_0 \oplus B_0$$

$$C_1 = A_0 \cdot B_0$$


## Half Adder

$$S = A \oplus B$$

$$C = A \cdot B$$

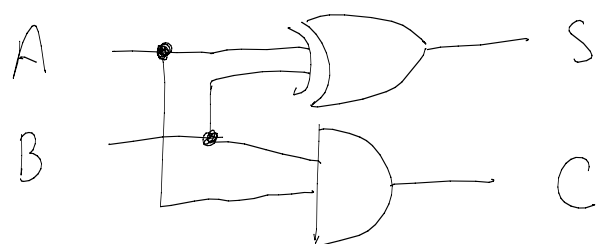

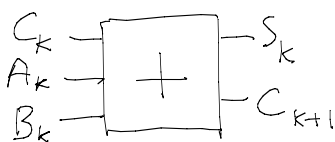
$$\begin{array}{r}
 C_{n-1} \dots C_2 C_1 C_0 \\
 A_{n-1} \dots A_2 A_1 A_0 \\
 B_{n-1} \dots B_2 B_1 B_0 \\
 \hline
 S_{n-1} \dots S_2 S_1 S_0
 \end{array}$$



Full adder

$A_k$	$B_k$	$C_k$	$S_k$	$C_{k+1}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

## Ripple Adder

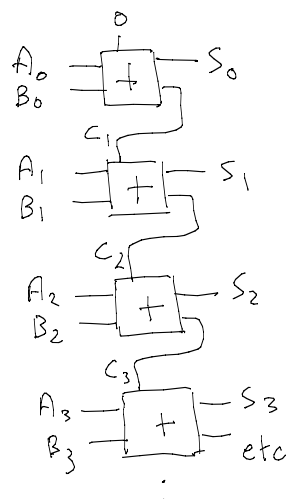


If  $n=32$ , we can have a long delay as carries propagate through the circuit.



We'll return to this later.

## Overflow

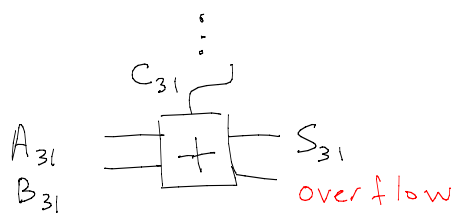

$A_{31}$	$B_{31}$	$S_{31}$	overflow
----------	----------	----------	----------

See Exercises 2

## Encoder

$A_m \dots A_2 A_1 A_0$	$Y_n \dots Y_0$

events  
(many bits)

code word  
(few bits)

## Encoder: Example 1

panel  
with  
five  
buttons



$b_4$	$b_3$	$b_2$	$b_1$	$b_0$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	1	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	1	0	0	0	0	1	1
1	0	0	0	0	1	0	0

Suppose only one pressed at any time

Q: What if two buttons are pressed at same time?

A: none of lights go on.  
(assuming a sum-of-products implementation of each  $L_i$ )

panel  
with  
five  
buttons




$b_4$	$b_3$	$b_2$	$b_1$	$b_0$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	0	0	0
x	x	x	x	1	0	0	1
x	x	x	1	0	0	1	0
x	x	1	0	0	0	1	1
x	1	0	0	0	1	0	0
1	0	0	0	0	1	0	1


Allow any number of buttons  
to be pressed.

## Encoder: Example 2

panel  
with  
ten  
buttons

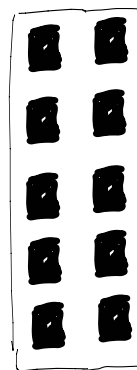

$b_9 \dots b_0$

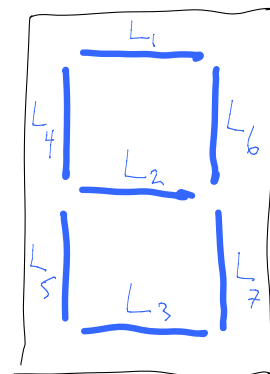

$b_9$	$b_0$	$L_7 L_6 \dots L_2 L_1$
0	1	0
1	0	0
1	1	0
1	1	0
1	1	0
1	1	0
1	1	0
1	1	0
1	1	0
1	1	0



see  
Exercises  
2

## Decoder


$b_2 b_1 b_0$	$Y_7$	$\dots$	$Y_2 Y_1 Y_0$
0 0 0	1		
0 0 1			0
0 1 0			
0 1 1			
1 0 0			
1 0 1			
1 1 0			
1 1 1			

code  
word

events

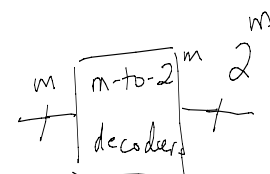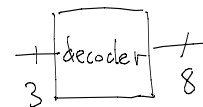


## Multiplexor (also called selector)

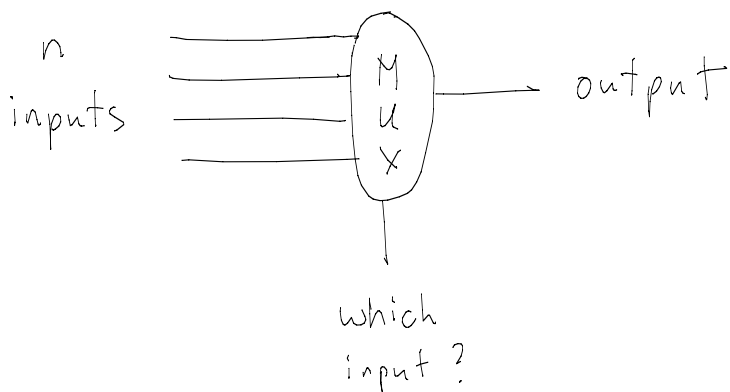


## 1-bit multiplexor


$$Y = \bar{S} \cdot A + S \cdot B$$

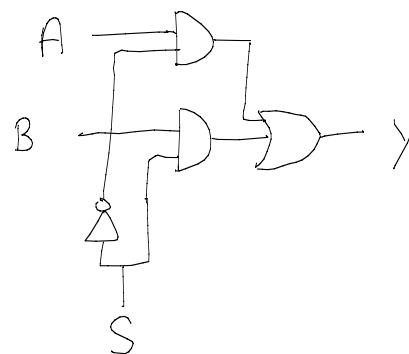

2-bit multiplexor (What is the circuit?)

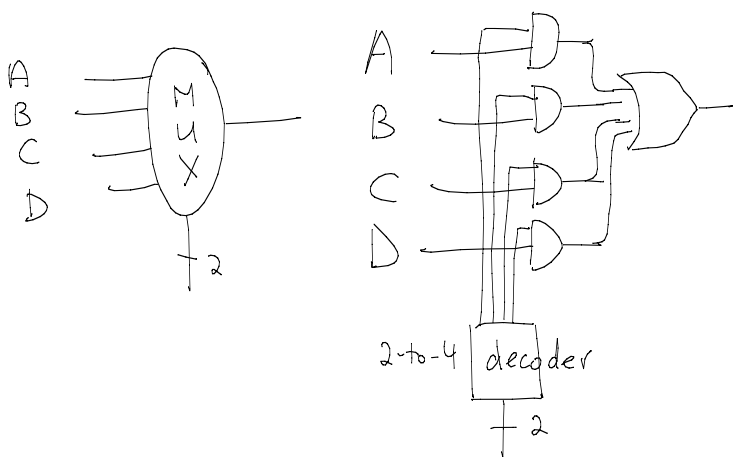

2-bit multiplexor

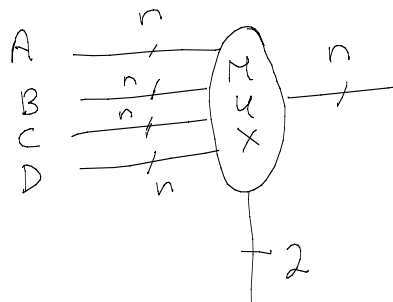


Selects from four  $n$ -bit inputs. For each  $A_i B_i C_i D_i$ , replicate circuit on previous slide (but use same decoder).


## Ripple Adder

Recall arithmetic circuit

slow!

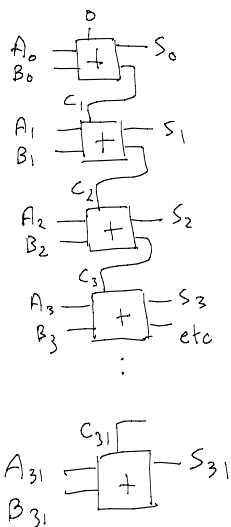


How to speed up the adder?

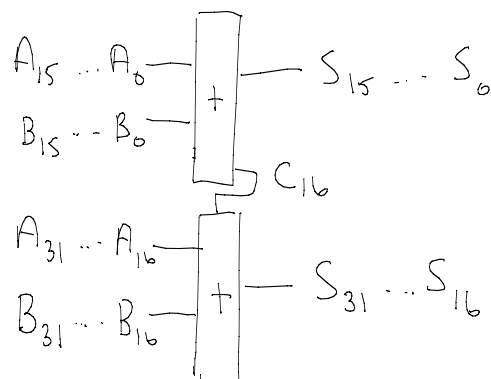

Does this speed it up? No.

## "Conditional Sum" Adder

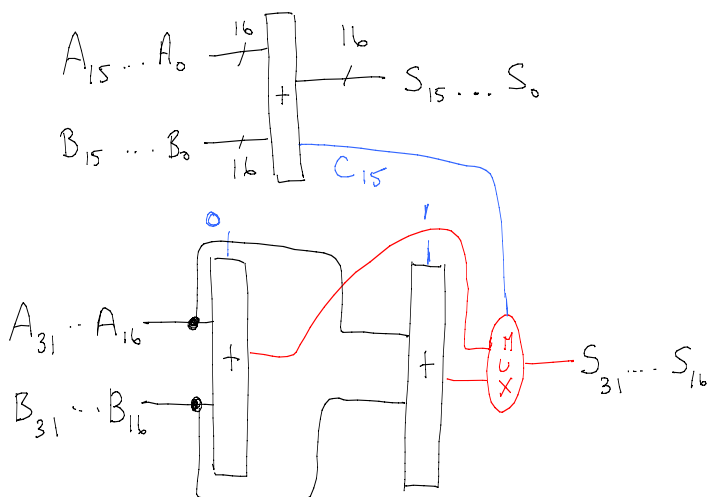

Many adders have been proposed:

small, slow




- ripple
  - ...
  - conditional sum (previous slide shows basic idea only)
  - ...
  - sum of products
- big, fast

## Subtraction

$$\begin{array}{r}
 A_{n-1} \dots A_2 A_1 A_0 \\
 - B_{n-1} \dots B_2 B_1 B_0 \\
 \hline
 S_{n-1} \dots S_2 S_1 S_0
 \end{array}$$


$$x - y = x + (-y)$$

$\uparrow$   
 invert bits and add 1

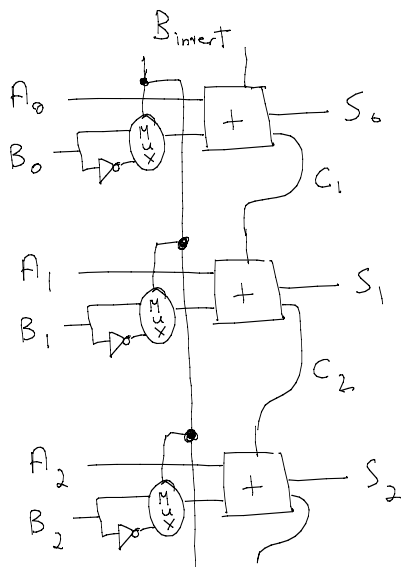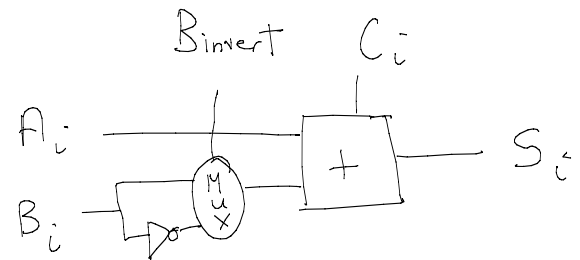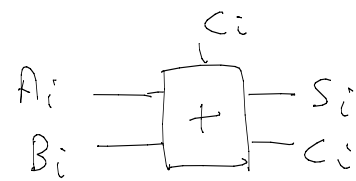


$$\begin{array}{r}
 A_{n-1} \dots A_2 A_1 A_0 \\
 - B_{n-1} \dots B_2 B_1 B_0 \\
 \hline
 S_{n-1} \dots S_2 S_1 S_0
 \end{array}$$

$n = 32$

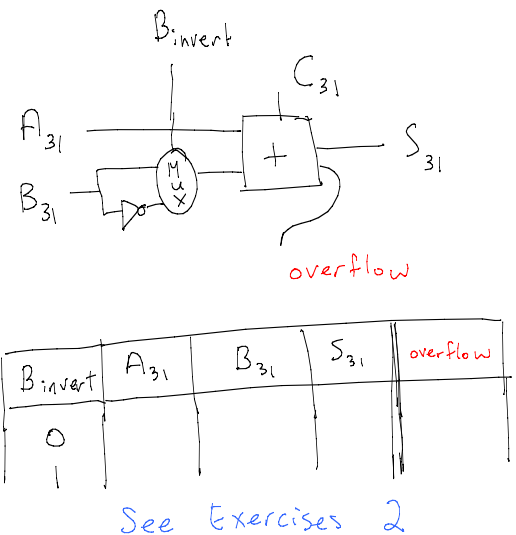

More operators:  
bit-wise AND, OR

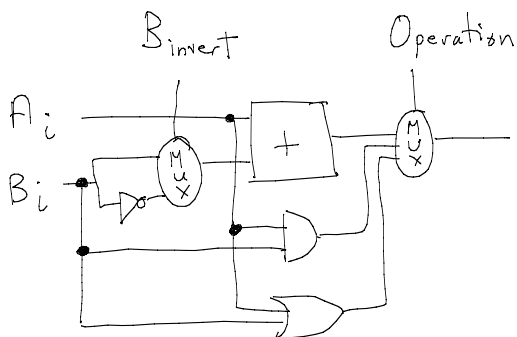

the fast adder implementation  
to the adder part

## Arithmetic Logic Unit (ALU)

